

**Name: Harsh Brahmecha**  
**20220802003**

**PRN:**

## **EXPERIMENT-2 (A)**

### **Aim:**

To design and implement Half & Full adders using logic gates for performing binary addition.

### **Requirements:**

- 1) Virtual Lab (Website)
- 2) MyDaq, Breadboard, Logic Gates or ICs and Wires (Hardware)
- 3) NI-ELVIS Mx (Software)

### **Theory:**

#### **Half Adder: -**

A half adder is a digital circuit that takes in two binary inputs, usually denoted as A and B, and produces two outputs: the sum (S) and the carry (C). The sum is the binary addition of A and B, while the carry is the bit that needs to be added to the next digit position. The truth table for a half adder is as follows:

The equations for the sum and carry outputs in a half adder are:

$$S = A \oplus B$$

$$C = A B$$

#### **Full Adder: -**

A full adder, on the other hand, takes in three binary inputs: A, B, and the carry-in ( $C_i$ ), and produces two outputs: the sum (S) and the carry-out ( $C_o$ ). The sum output is the binary addition of A, B, and  $C_i$ , while the carry-out is the bit that needs to be added to the next digit position. The truth table for a full adder is as follows:


The equations for the sum and carry outputs in a full adder are:

$$S = A \oplus B \oplus C_i$$

$$C_o = (A B) + (A C_i) + (B C_i)$$


### **Circuit Diagram:**

**Half Adder Circuit Diagram:**

 

In the above circuit diagram, the two input variables are A and B, and the two output variables are S (sum) and C (carry).

#### **Full Adder Circuit Diagram:**

 

In the above circuit diagram, the three input variables are A, B, and  $C_i$  (carry-in), and the two output variables are S (sum) and  $C_o$  (carry-out).

#### **Observation Table:**

##### **I. Half Adder**

Input Variables- A, B  
Output Variables- S, C  
Where S represents Sum,  
C represents Carry.

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

**Output:** Attach the screenshots of the simulation of half adder done on MyDAQ.



## II. Full Adder

Input Variables- A, B, Ci  
Output Variables- S, Co  
where S represents Sum and Co represents Carry out



A	B	Ci	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Output:**

**Half Adder: -**

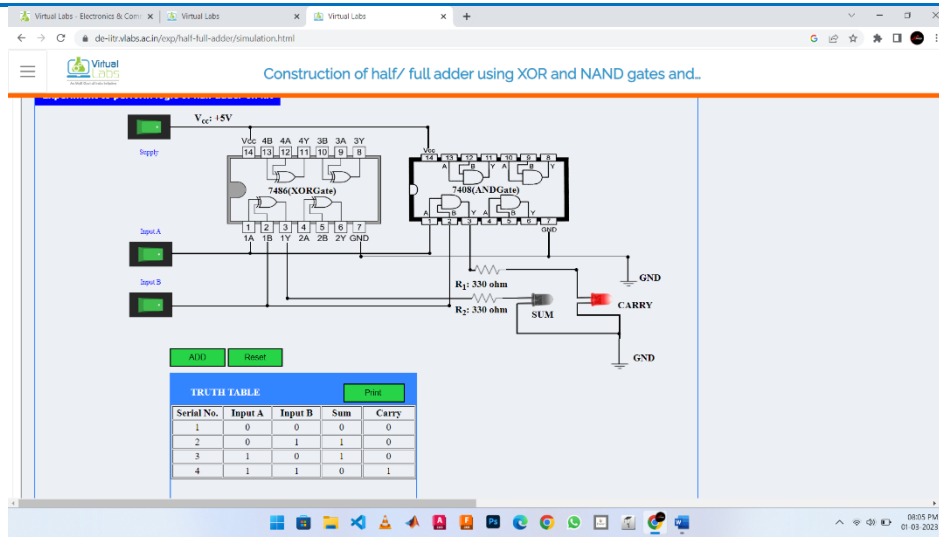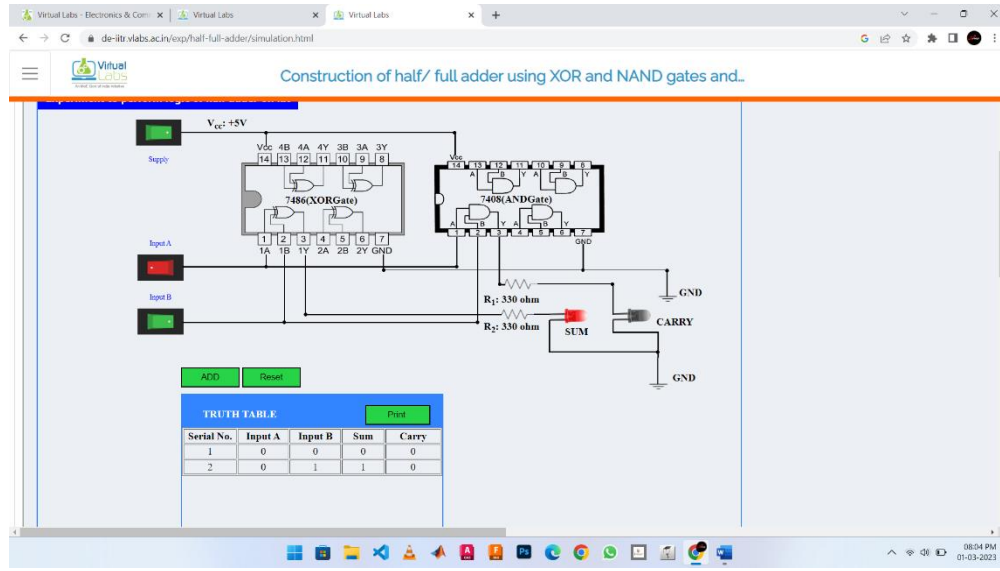

**Full Adder: -**

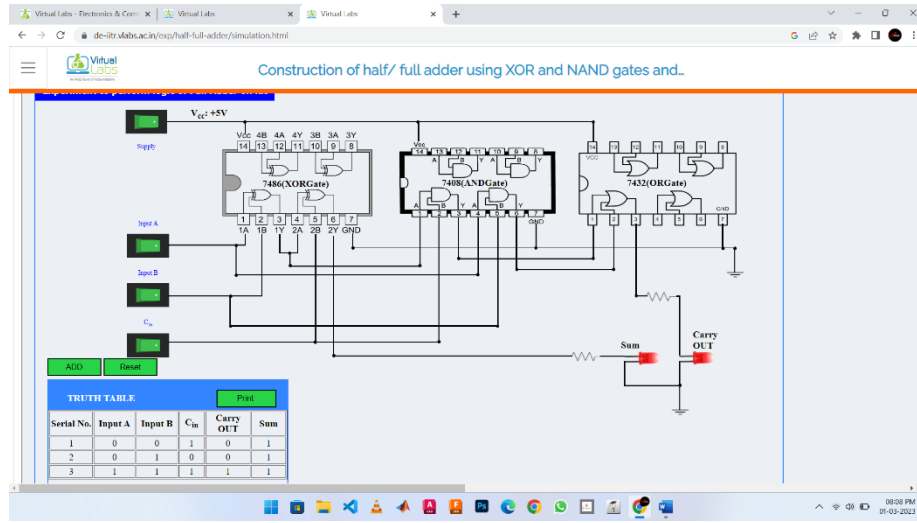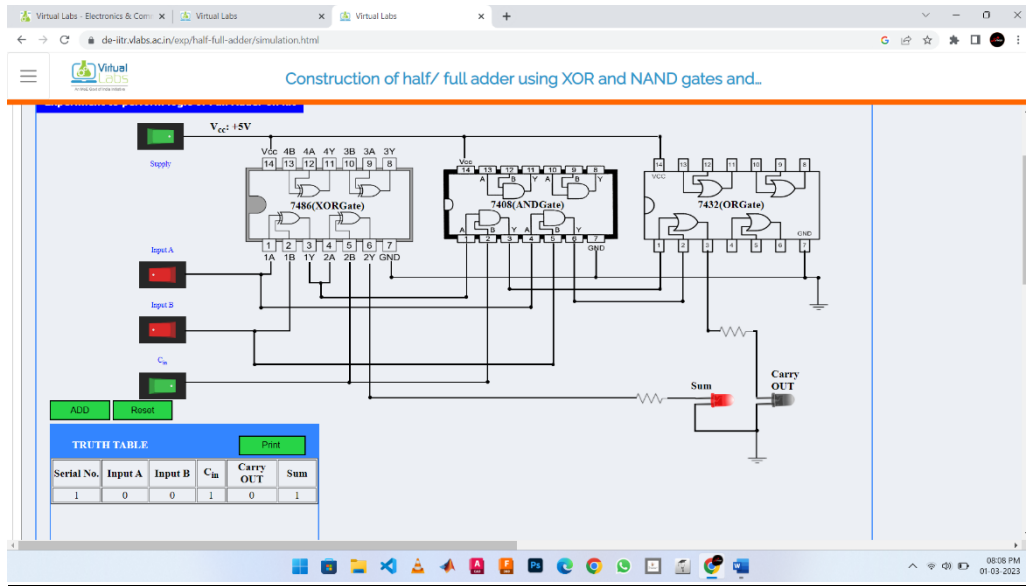

## Result:

Designing and implementation of Half & Full adders using logic gates for performing binary addition is done.

## **XPERIMENT-2 (B)**

### **Aim:**

To design and implement Half & Full subtractor using logic gates to perform binary subtraction.

### **Requirements:**

- 1) Virtual Lab (Website)
- 2) MyDaq, Breadboard, Logic Gates or ICs and Wires (Hardware)
- 3) NI-ELVISmx (Software)

### **Theory:**

#### **Half Subtractor: -**

A half subtractor is a combinational circuit that subtracts two bits and produces the difference and borrow as outputs. The circuit takes two inputs A and B, and produces two outputs, the difference D and borrow-out (Bo).

The equations for difference (D) and borrow (Bo) are:

$$D = A \oplus B$$

$$Bo = A'B$$

#### **Full Subtractor: -**

A full subtractor is a combinational circuit that subtracts three binary bits, the minuend, subtrahend, and borrow-in, and produces the difference and borrow-out as outputs. The circuit takes three inputs A, B, and (Bi) and produces two outputs, the difference D and borrow-out (Bo).


The equations for difference (D) and borrow (Bo) are:

$$D = A \oplus B \oplus Bi$$

$$Bo = (A'B + Bi'A)$$


### **Circuit Diagram:**
 
#### **Half Subtractor Circuit Diagram:**



In the above circuit diagram, the two input variables are A and B, and the two output variables are D (difference) and Co (carry).

### Full Subtractor Circuit Diagram:

 

In the above circuit diagram, the three input variables are A, B, and Bi (borrow-in), and the two output variables are D (difference) and Bo(borrow-out).

### Observation Table:

#### I. Half Subtractor

Input Variables- A, B

Output Variables- D, B<sub>out</sub>

Where D represents Difference,

B<sub>out</sub> represents Borrow.

A	B	S	C
0	0	0	0
0	1	1	1

1	0	1	0
1	1	0	0

**Output:** Attach the screenshots of the simulation of half subtractor done on MyDAQ.

## II. Full Subtractor

Input Variables- A, B, B<sub>in</sub>

Output Variables- D, B<sub>out</sub>


Where, D represents Difference,

B<sub>out</sub> represents Borrow


A	B	Ci	S	Co
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

**Output: -**


**Half Subtractor: -**

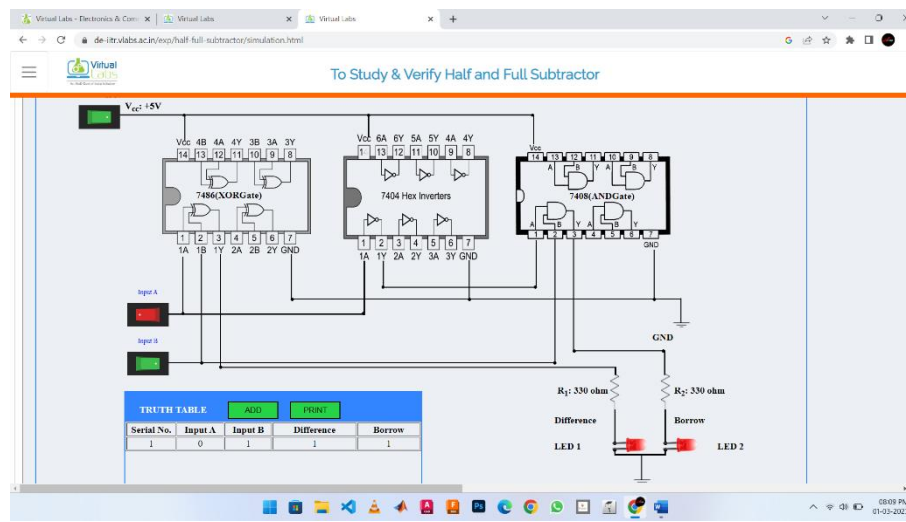




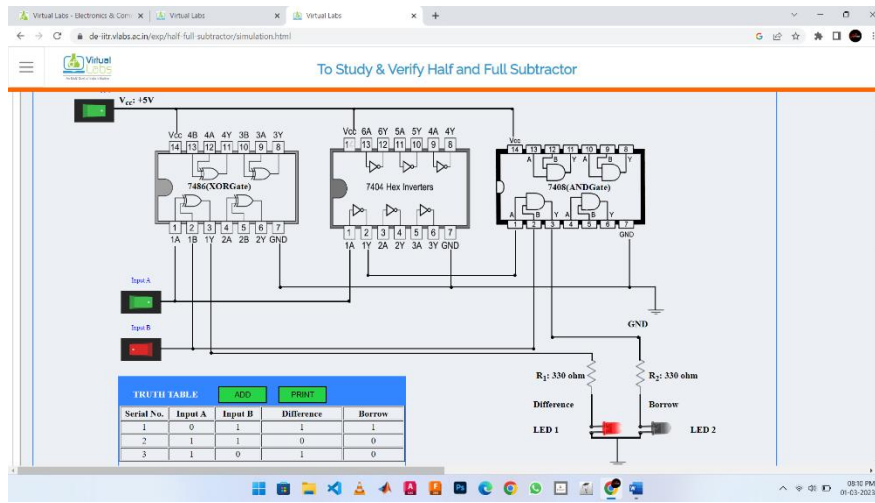

## Full Subtractor: -

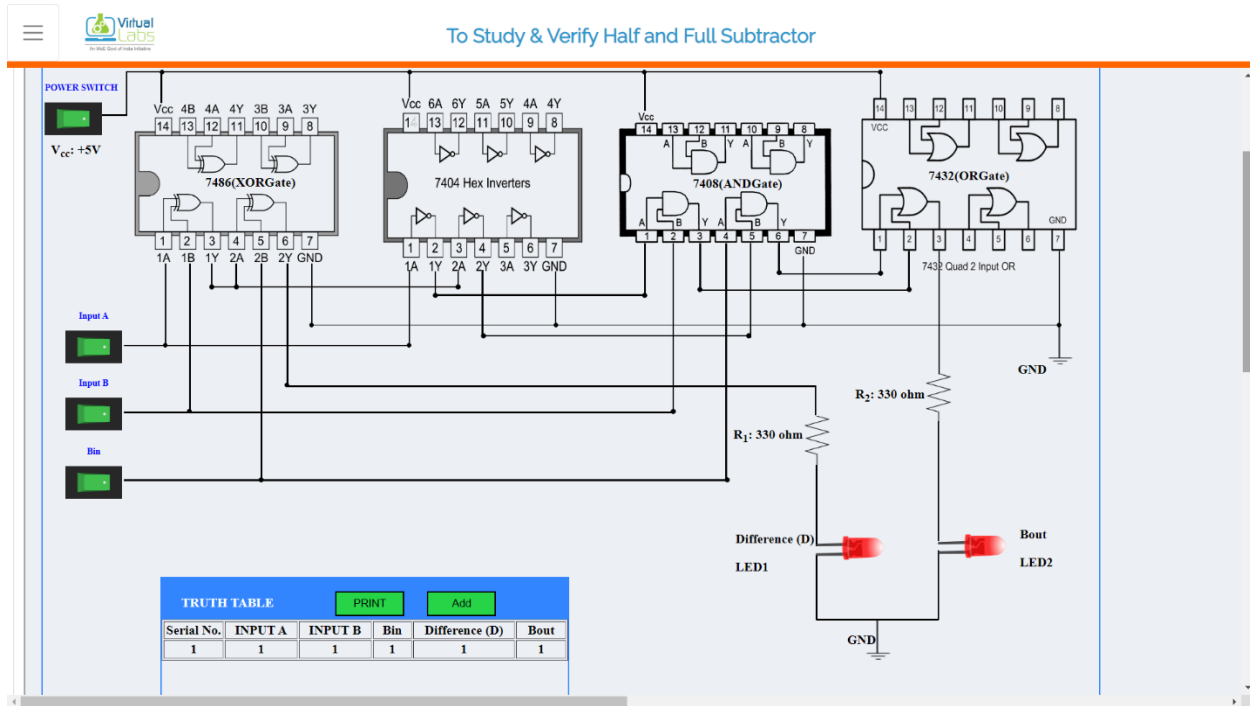

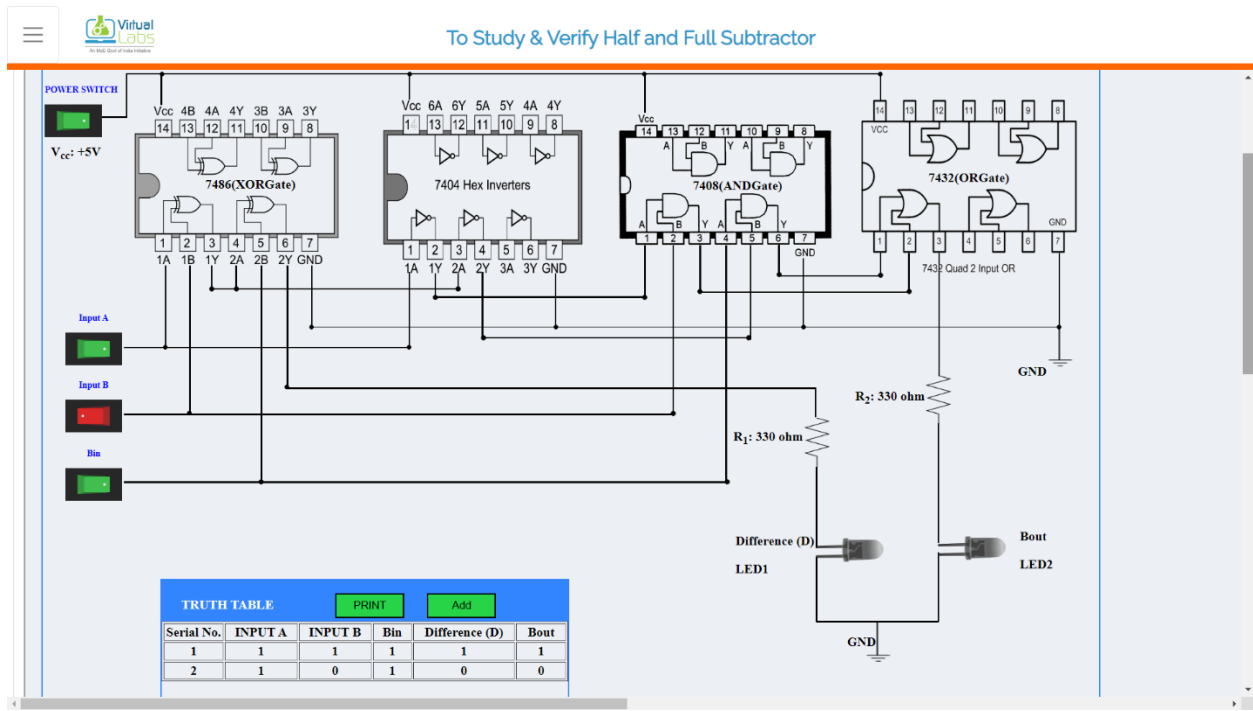

### **Result:**

Designing and implementation of Half & Full subtractor using logic gates for performing binary subtraction is done.